

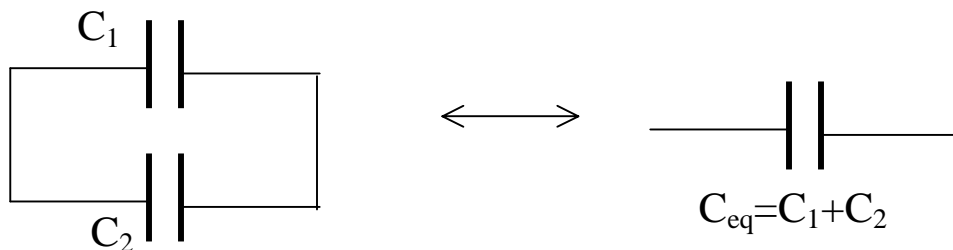
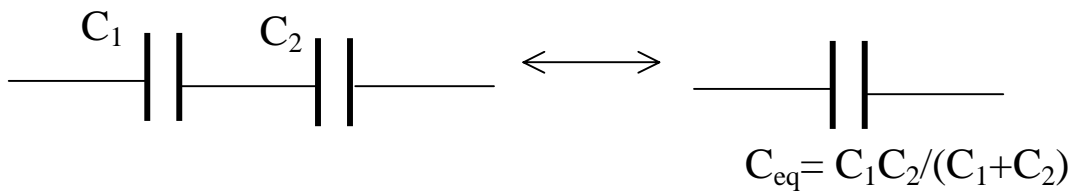
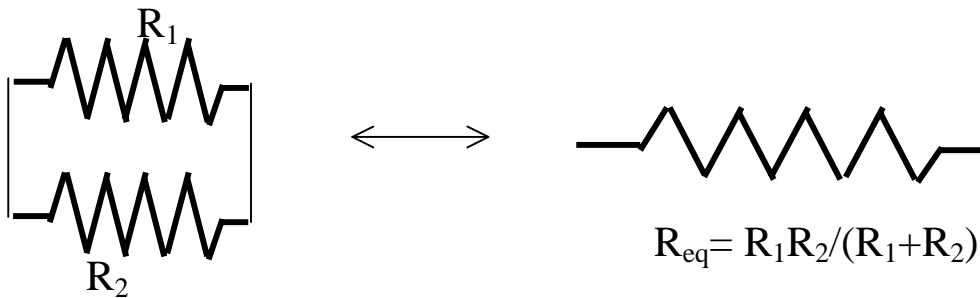


Homework 7

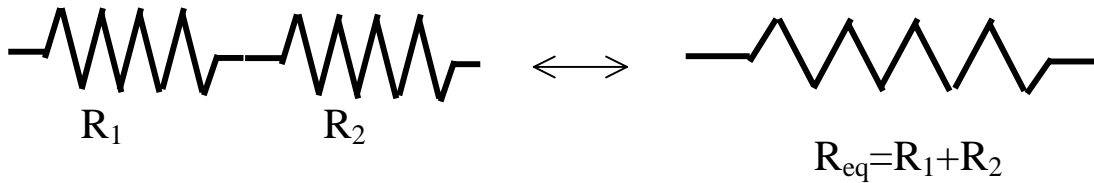1. [4 points] Show that the following circuit segments shown on the left can be simplified to the ones shown on the right.



2. Consider the circuit shown below.

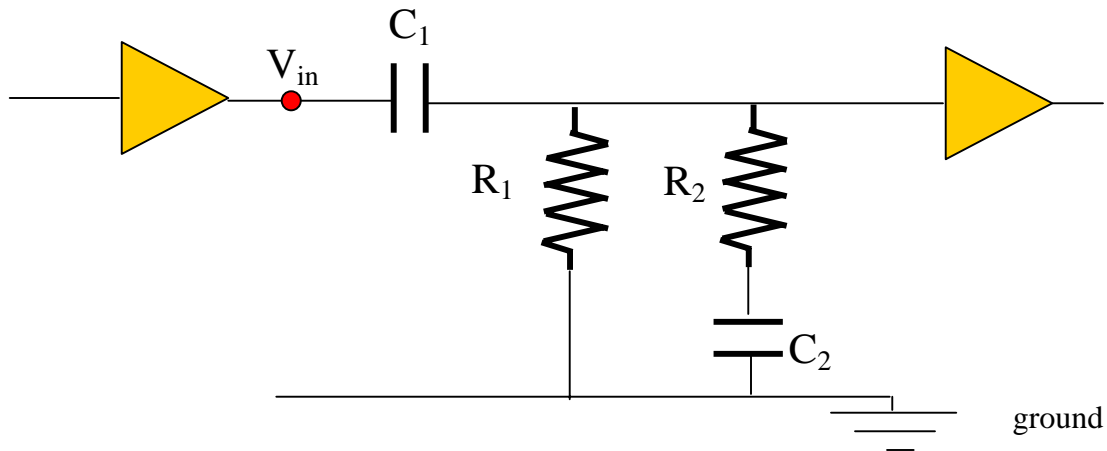


(2.i) [8 points] The capacitors in this circuit are initially uncharged when the switch is closed at time $t=0$. Systematically analyze this circuit to obtain the state equations for the voltages across the two capacitors in the form: $\dot{\mathbf{X}} = \mathbf{A}\mathbf{X} + \mathbf{F}$. Adapt a MATLAB code to solve this state equation.

(2.ii) [2 points] Given: $V_{in}(t) = 1.6\text{kV}$ constant, $C_1=C_2=8.5\mu\text{F}$, $R_1=R_2=0.5\text{M}\Omega$ plot the voltages across the two capacitors as a function of time. Qualitatively explain the behavior.

(2.iii) [4 points] Given $V_{in}(t) = 1.6\text{kV} \cdot \sin(\omega_f t)$ where ω_f is the angular frequency of the input signal; $C_1=C_2=6.5\mu\text{F}$, $R_1=R_2=0.73\text{M}\Omega$ plot the voltages across the two capacitors as a function of time for values of ω_f equal to 0.5/s, 2/s, 4/s. Qualitatively describe the behavior.

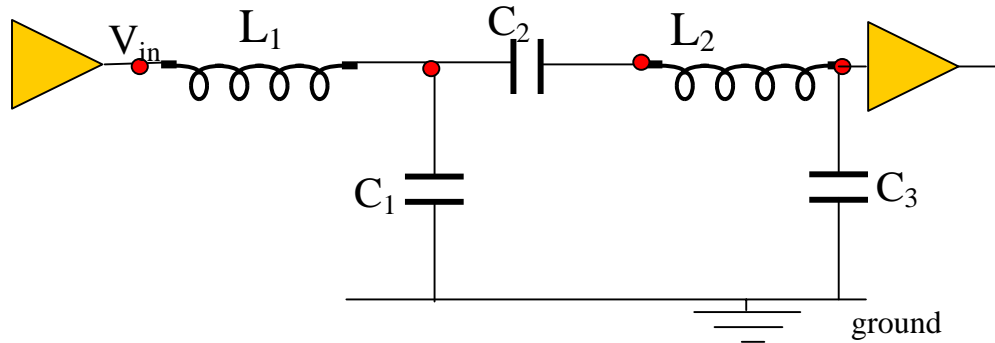3. Consider the circuit shown below. It consists of two LC-oscillators that are coupled together by a capacitor.



(3.i) What are the state variables for this circuit? [2 points]

(3.ii) Systematically obtain the first-order state equations in the form: $\dot{\mathbf{X}} = \mathbf{A}\mathbf{X} + \mathbf{F}$ [4 points]

(3.iii) Adapt a MATLAB code to analyze this circuit. Make sure that your code can plot the total energy in the left oscillator (L1-C1) and the right oscillator (L2-C3). Let the input voltage V_{in} be a constant value applied for the first 4 seconds only and then zero thereafter. By using appropriate values for the capacitances and inductances, get this circuit to “slosh” similar to weakly-coupled mechanical oscillators. Show the sloshing behavior by means of time plots of energy in the left and right oscillators. [6 points]